



# **Battery Charger with MPPT Reference Design**

**MP2731 – Single-Cell Switching Charger with MC96F1206**



## Contents

1	Overview .....	0
1.1	Description .....	0
1.2	Features .....	0
1.3	Applications .....	0
2	Reference Design .....	3
2.1	Block Diagram .....	3
2.2	Related Solutions .....	3
2.3	System Specifications .....	3
3	Design .....	4
3.1	MP2731 Single-Cell Switching Charger .....	4
3.1.1	Inductor Selection .....	4
3.1.2	System Capacitor Selection .....	4
3.2	MPPT Algorithm .....	<b>Error! Bookmark not defined.</b>
3.2.1	MPPT Theory .....	<b>Error! Bookmark not defined.</b>
3.2.2	MPPT Software Implementation .....	6
3.3	Schematic .....	8
3.4	BOM .....	9
3.5	PCB Layout .....	0
4	Test Results .....	1
4.1	Charging Efficiency .....	1
4.2	Time Domain Waveforms .....	0
5	Start-Up .....	0
6	Disclaimer .....	0

## 1 Overview

### 1.1 Description

In an era characterized by the internet of things (IoT), more connectivity means more outdoor devices are now battery-powered and constantly communicating. In particular, there is an increasing number of outdoor devices being powered through solar panels. This reference design is for maximum power point tracking (MPPT) in outdoor designs with a solar panel. It illustrates design tips for a solar panel charger with a Lithium-ion battery, and is suitable for applications such as outdoor solar surveillance cameras or outdoor lighting.

This reference design is developed based on the MP2731, a single-cell switching charger IC from MPS, and the MC96F1206 controller (a low-cost 8051 MCU). It is suitable for small and medium solar-powered charging solutions. The MP2731 integrates a VIN connection switcher, ADC, and voltage/current-sense circuit, which significantly reduce system size and cost. This reference design uses the perturb-and-observe (P&O) algorithm for MPPT to achieve a minimum 98% tracking accuracy.

### 1.2 Features

- Wide 3.7V to 16V Operating Input Range
- Up to 22V Sustainable Input Voltage
- Up to 4.5A Charge Current
- Up to 93% Charge Efficiency in 9V Input 5W System
- Up to 98% MPPT Accuracy
- Low to 41.5 $\mu$ A Battery Current in Standby Mode
- Low to 13 $\mu$ A Battery Current in Shipping Mode
- NVDC PPM to Support System Instant-On and Battery Supplement
- I<sup>2</sup>C Interface for Flexible System Parameter Setting and Status Reporting
- Robust Charging Protections, including Configurable JEITA and Safety Timer
- Available in a 25mmx25mm Core Circuit Area

### 1.3 Applications

- Outdoor Solar Surveillance Cameras
- Outdoor Lighting
- E-Bike Battery Chargers

 


Figure 1: Evaluation Board

All MPS parts are lead-free and adhere to the RoHS directive. For MPS green status, please visit the MPS website under Quality Assurance. "MPS", the MPS logo, and "Simple, Easy Solutions" are registered trademarks of Monolithic Power Systems, Inc. or its subsidiaries.



**Warning:** Although this board is designed to satisfy safety requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolation transformer to provide the AC input to the prototype board.

## 2 Reference Design

### 2.1 Block Diagram

Figure 2 shows the system block diagram for this reference design.

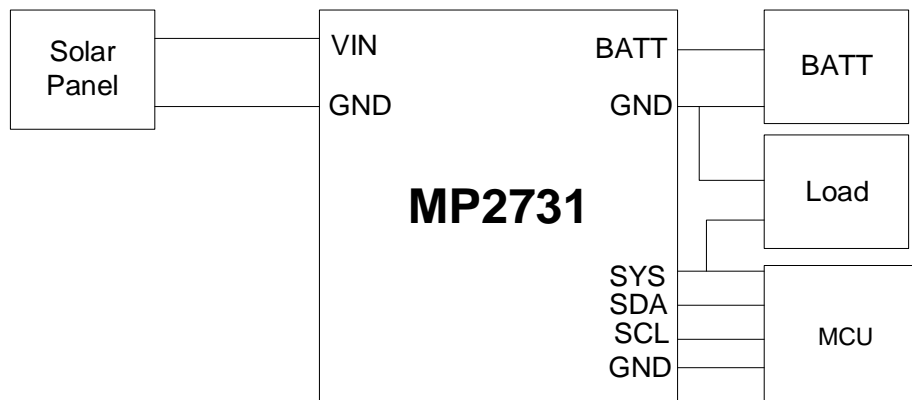


Figure 2: Block Diagram

### 2.2 Related Solutions

This reference design is based on the following MPS solution:

Table 1: System Specifications

MPS Integrated Circuit	Description
MP2731	Single-cell switching charger with I <sup>2</sup> C control and NVDC PPM

### 2.3 System Specifications

Table 2: System Specifications

Parameter	Specification
Input voltage range	3.7V to 16V
System output voltage	Up to $V_{BATT}$ (about 3.6V) + 100mV
System output current	Up to 4.5A
Charge current	Up to 4.5A
Switching frequency	1350kHz
Board form factor	63mmx63mmx3mm

### 3 Design

#### 3.1 MP2731 Single-Cell Switching Charger

The MP2731 is a 4.5A, highly integrated, switch-mode battery charger with NVDC power path management for a single-cell Li-ion or Li-polymer battery.

##### 3.1.1 Inductor Selection

Inductor selection is a tradeoff between cost, size, and efficiency. From a practical standpoint, the inductor ripple current should not exceed 30% of the maximum load current under worst-case conditions. If the MP2731 operates with a 5V input voltage, the maximum inductor current ripple occurs after pre-charge, and when constant current (CC) charge begins. The inductance can be estimated with Equation (1):

$$L = \frac{V_{IN} - V_{SYS}}{\Delta I_{L\_MAX}} \frac{V_{SYS}}{V_{IN} \times f_{SW} \text{ (MHz)}} (\mu\text{H}) \quad (1)$$

Where  $V_{IN}$  is the input voltage,  $V_{SYS}$  is the system voltage,  $f_{SW}$  is the switching frequency, and  $\Delta I_{L\_MAX}$  is the maximum inductor ripple current, which is about 30% of the CC charge current.

The peak current can be calculated with Equation (2):

$$I_{PEAK} = I_{LOAD(MAX)} \times \left(1 + \frac{\% \text{ripple}}{2}\right) (\text{A}) \quad (2)$$

The MP2731 has a maximum charge current of 4.5A, but the actual charge current cannot reach this value for the input current limit. For most applications, the maximum inductor current ripple is set to 0.5A with a 5V input voltage, so the inductor is 1.5 $\mu$ H. For small applications, select a 1.0 $\mu$ H inductor with a low DC resistance to optimize efficiency.

##### 3.1.2 System Capacitor Selection

To ignore the ESR of the output capacitor, use a small ceramic capacitor with a lower ESR. The output voltage ripple can then be estimated with Equation (3):

$$\Delta r = \frac{\Delta V_{SYS}}{V_{SYS}} = \frac{1 - \frac{V_{SYS}}{V_{IN}}}{8 \times C_{SYS} \times f_{SW}^2 \times L} \% \quad (3)$$

To guarantee the  $\pm 0.5\%$  system voltage accuracy, the maximum output voltage ripple must not exceed 0.5% (e.g. 0.1%). The maximum output voltage ripple occurs at the minimum system voltage and the maximum input voltage.

If  $V_{IN} = 5\text{V}$ ,  $V_{SYS} = 3.7\text{V}$ ,  $L = 1\mu\text{H}$ ,  $f_{SW} = 1.35\text{MHz}$ , and  $\Delta r = 0.1\%$ , the output capacitor can be calculated with Equation (4):


$$C_{SYS} = \frac{1 - \frac{V_{SYS}}{V_{IN}}}{8 \times f_{SW}^2 \times L \times \Delta r} \quad (4)$$

In this example, choose a 22 $\mu$ F ceramic capacitor.

### 3.2 MPPT Algorithm

#### 3.2.1 MPPT Theory

The output power from a solar panel is determined by several factors: the irradiance level, the operating voltage and current of the panel, and the load. There is a maximum power point where the solar panel outputs optimal power to the system (see Figure 3). Maximum power point tracking techniques, such as perturb-and-observe (P&O) or incremental conductance methods, ensure that the solar panels operate at MPPT under conditions where the irradiance changes.

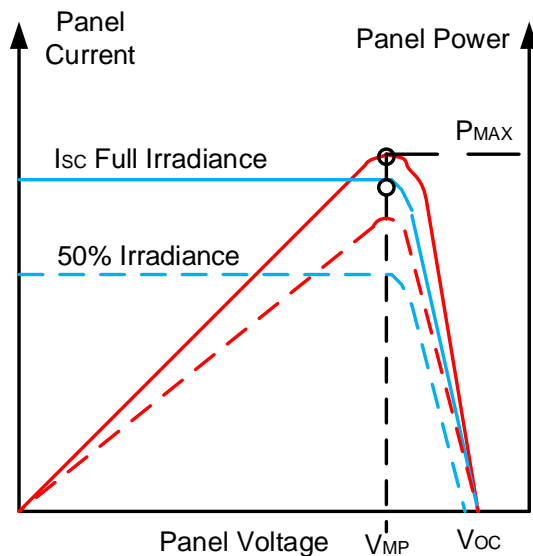

**Figure 3: Solar Panel P-V and I-V Curve**


In the power-based P&O MPPT algorithm, the power-to-voltage derivative ( $dP_o/dV_o$ ) of a solar panel is used as a tracking parameter. Calculate when MPP is reached using Equation (5):

$$\frac{dP_o}{dV_o} = 0 \quad (5)$$

Where  $P_o$  is solar panel output power,  $V_o$  is solar panel output voltage.

### 3.2.2 MPPT Software Implementation

The P&O MPPT algorithm is implemented in a 20-pin, 8-bit MC96F1206 MCU from ABOV Semiconductor. To communicate with the MP2731, the I<sup>2</sup>C peripherals in the MCU are activated. Figure 4 shows the system-level software flow.

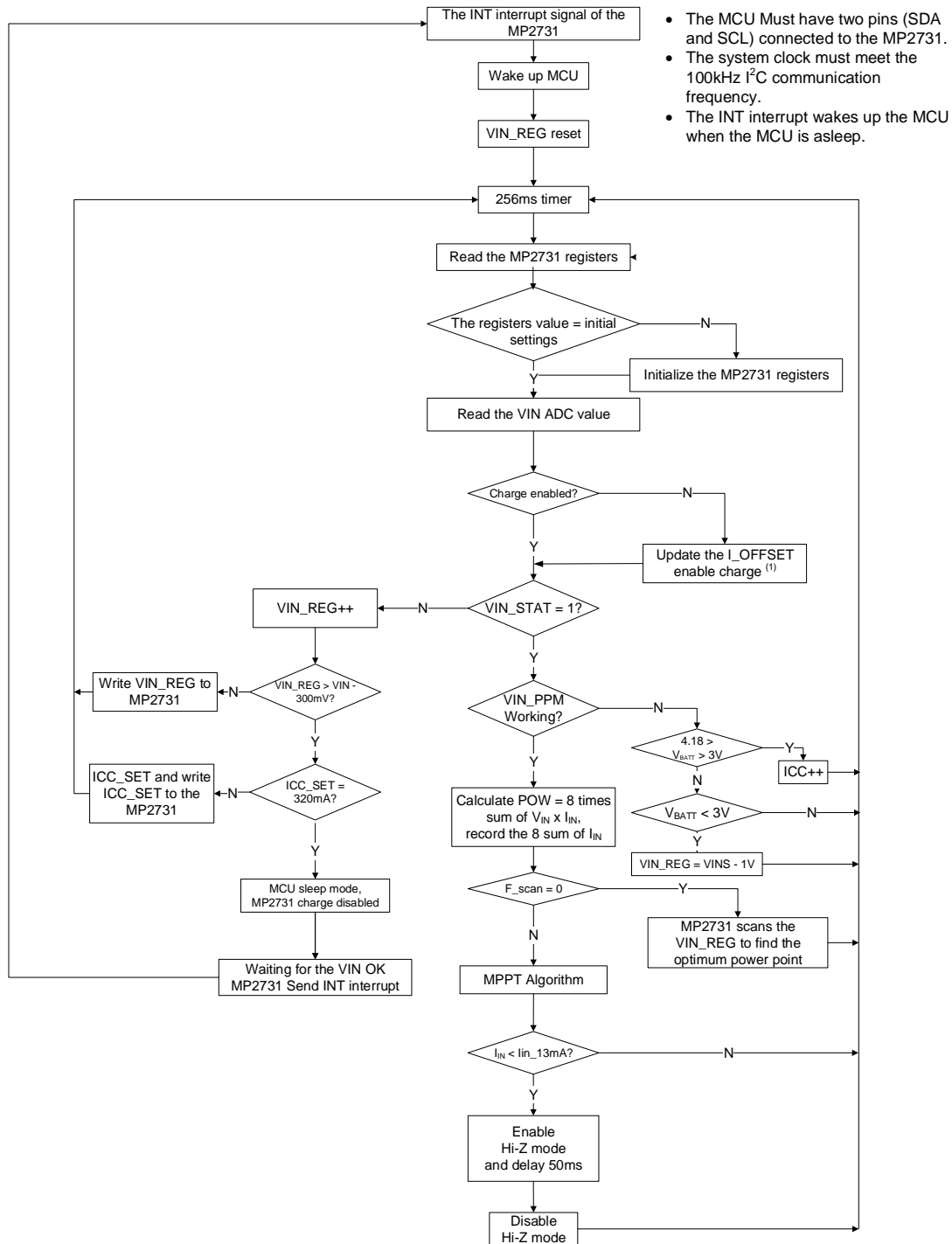

**Figure 4: System-Level Software Flowchart**

**Note:**

- 1) Before updating I\_OFFSET, turn off other devices connected at the MP2731's SYS pin to ensure that I\_OFFSET is calibrated correctly.

The MCU enters sleep mode if  $V_{IN}$  experiences an input power failure. If  $V_{IN}$  is sufficient, the INT interrupt signal is sent to wake up the MCU. Then the MCU reads the MP2731 registers and initiates the registers (see Table 1).

**Table 1: Operation Registers**

Register Address	Value (Hex)	Value (Bin)	Description
0x00	0x7F	0111 1111	Sets the input current limit to 3.25A (maximum).
0x02	0xDC	1101 1100	Automatic input current optimization is disabled.
0x03	0x50	0101 0000	ADC continuous conversion is enabled.
0x08	0x84	1000 0100	Termination is enabled, and WTD and safety time are disabled.
0x0B	0xC0	1100 0000	USB detection is disabled.


By setting the input current limit to its maximum value, the panel voltage is controlled only by the input voltage limit loop. By adjusting the input voltage limit loop reference, the PV panel's voltage can be adjusted. After initializing the MP2731, read the ADC initial value, and then enable charging.

If  $VIN\_STAT$  is not equal to 1, increase  $VIN\_REG$  by one unit, and then continue to go back to the previous  $VIN\_STAT$  value. If  $VIN\_REG$  reaches its maximum limit and  $VIN\_STAT$  is still is not equal to 1, gradually decrease the charging current and return to the previous  $VIN\_STAT$  value.

If  $VIN\_REG$  set has reached its limit, the ICC set has a minimum at the same time. However, if  $VIN\_STAT$  still is not equal to 1, the MCU goes into sleep mode. Meanwhile, the MP2731's charging is disabled until the INT interrupt wakes the MCU.

If the PV panel is partially covered and a local MPP can be tracked using a conventional P&O MPPT algorithm, then the MCU initiates a scan every time the input voltage flag changes. To find the optimal power point, the MCU adjusts the input regulation voltage reference of the MP2731 with a 100mV step from 50% of the panel's open-circuit voltage ( $V_{OC}$ ) to 80% of  $V_{OC}$ .

After the initial scan, the PV panel operates at the maximum power point. To continue tracking the optimal point under varying load and irradiance conditions, the P&O algorithm runs every 256ms on the MCU (see Figure 5).

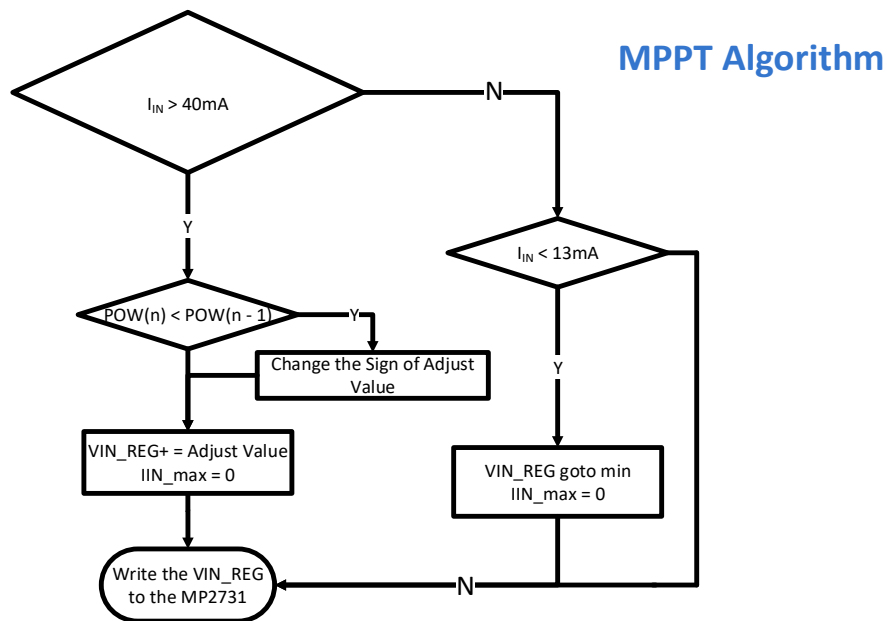

**Figure 5: P&O MPPT Algorithm**



### 3.3 Schematic

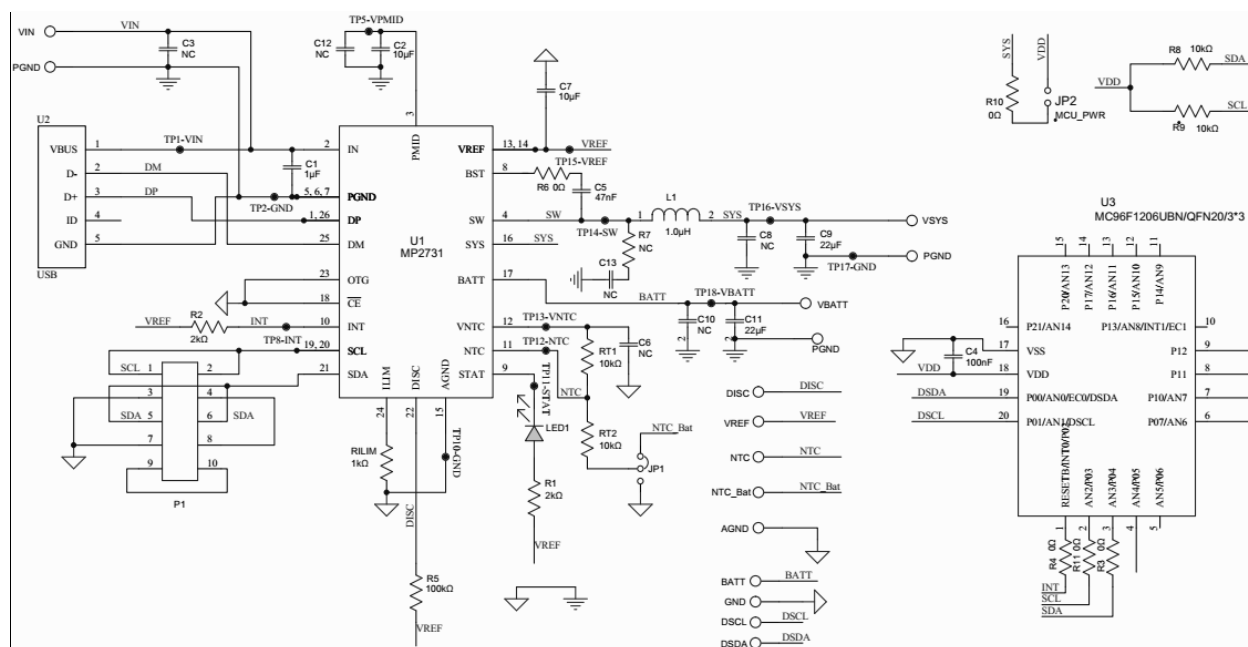


Figure 6: Battery Charger with MPPT Schematic

### 3.4 BOM

Qty	Ref	Value	Description	Package	Manufacturer	Manufacturer P/N
1	C1	1 $\mu$ F	Ceramic capacitor, 25V, X7R	0603	Murata	GRM188R71E105KA12D
1	C2	10 $\mu$ F	Ceramic capacitor, 50V, X5R	1206	Murata	GRM31CR61H106KA12L
1	C4	100nF	Ceramic capacitor, 25V, X5R	1206	Murata	GCM188R71C104KA37D
1	C5	47nF	Ceramic capacitor, 25V, X5R	0603	Murata	GRM188R71H473KA61D
1	C7	10 $\mu$ F	Ceramic capacitor, 16V, X5R	0603	Murata	GRM188R61C106KAALD
2	C9, C11	22 $\mu$ F	Ceramic capacitor, 10V, X7R	1206	Murata	GRM31CR71A226KE15L
1	C3	NC	Ceramic capacitor,	1206		
1	C12	NC	Ceramic capacitor,	0805		
4	C6, C8, C10, C13	NC	Ceramic capacitor,	0603		
1	L1	1 $\mu$ H	Inductor, 1 $\mu$ H, 21m $\Omega$ , 7A	SMD	Cyntec	HTEP32251B-1R0MIR-89
1	LED1		Red LED	0805	Bright LED	BL-HUF35A-TRB
2	R1, R2	2k $\Omega$	Film resistor, 1%	0603	Yageo	RC0603FR-072KL
1	R1LIM	1k $\Omega$	Film resistor, 1%	0603	Yageo	RC0603FR-071KL
4	RT1, RT2, R8, R9	10k $\Omega$	Film resistor, 1%	0603	Yageo	RC0603FR-0710KL
5	R3, R4, R6, R10, R11	0 $\Omega$	Film resistor, 1%	0603	Yageo	RC0603FR-070RL
1	R5	100k $\Omega$	Film resistor, 5%	0603	Yageo	RC0603JR-07100KL
1	R7	NC	Film resistor,	0603		
2	JP1, JP2		2.54mm connector			
2	JP1, JP2		2.54mm short			
1	P1		Header, 5-pin, dual row			
10	GND, DISC, NTC, INT, VREF, NTC_BAT, BATT, GND, DSCL, DSDA		2.54mm connector			



## Battery Charger with MPPT Reference Design


### MP2731 – Single-Cell Switching Charger with MC96F1206

6	VIN, PGND, VBATT, PGND, PGND, VSY5		2mm pin			
11	GND, VPMID, DP, DM, VIN, VBATT, VSY5, GND, SW, BST, STAT		Test point			
1	U1	MP2731GQC-0001	I <sup>2</sup> C-controlled switching charger with NVDC power path and USB OTG	QFN-26 (3.5mmx3.5mm)	MPS	MP2731GQC-0001
1	U2	NC	Micro-B USB receptacle	7.5mmx2.45mmx5mm		
1	U3		MCU	QFN-20 (3mmx3mm)	ABOV	MC96F1206USBN

### 3.5 PCB Layout

PCB layout is critical for stable operations. For the best results when designing the general switching design, refer to Figure 7 and follow the guidelines below:

1. Route the power stage adjacent to ground.
2. Minimize the high-side switching node (SW, inductor) trace lengths in both the high-current paths and the current-sense resistor trace.
3. Keep the switching node short and route it away from all small control signals, especially the feedback network.
4. Place the input capacitor as close as possible to the PMID and PGND pins.
5. Place the output inductor close to the IC, and connect the output capacitor between the inductor and PGND of the IC.
6. For high-current applications, the pins for the power pads (IN, SW, SYS, BATT, and PGND) should be connected to as much copper in the board as possible. This improves thermal performance because the board conducts heat away from the IC.
7. Connect a ground plane directly to the return of all components through via holes.
8. If possible, place via holes inside the PGND pads for the IC.
9. It is recommended to use a star ground design approach to keep circuit block currents isolated (high-power/low-power, small-signal), which reduces noise coupling and ground-bounce issues. A single ground plane for this design gives good results. With this small layout and a single ground plane, there is no ground bounce issue, and having the components segregated minimizes coupling between signals and stability requirements.
10. Pull the connect wire from the MCU (I<sup>2</sup>C) far from the SW mode and copper areas.
11. Place SCL and SDA in close parallel.

 


**Figure 7: Recommended PCB Layout Top Layer (Red) and Bottom Layer (Blue)**

## 4 Test Results

### 4.1 Charge Efficiency

**Figure 8: Charging Efficiency (5V Panels with Different Power)**

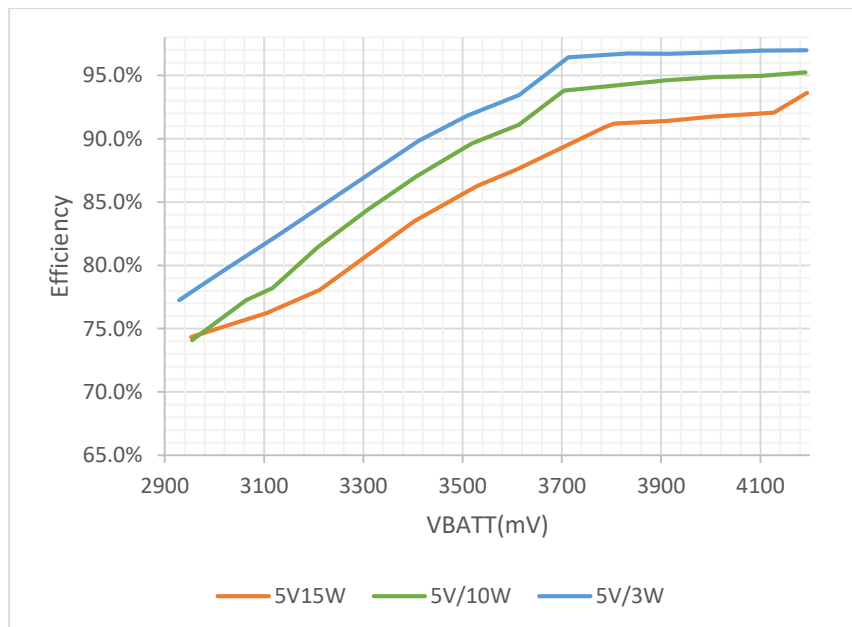

**Figure 9: Charging Efficiency (9V Panels with Different Power)**


 


Figure 10: Charge Efficiency (12V Panels with Different Power)

 

### 4.2 Time Domain Waveforms

Figure 11: MPPT Process for PV Panel from Start-Up to Steady State

 


Figure 12: MPPT Behavior during Charging Profile

 


Figure 13: Tracking Performance for Panel when Partially Shaded and when Shade Removed (5V Panel)



 



Figure 14: Tracking Performance for Panel when Partially Shaded and when Shade Removed (8V Panel)

 

**Figure 15: Tracking Performance for Solar Irradiance Changing (5V Panel)**

 

**Figure 16: Tracking Performance for Solar Irradiance Changing (8V Panel)**

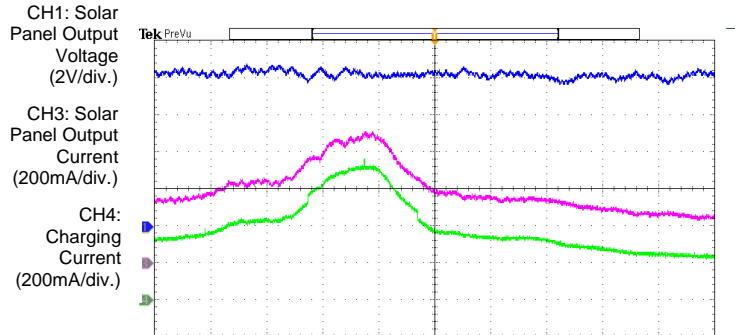

## 5 Start-Up

Follow the steps below for start-up:

1. Connect JP2.1 to JP2.2.
2. Connect the battery terminals to:
  - a) Positive (+): VBATT terminal
  - b) Negative (-): PGND terminal
3. Connect the solar panel to the IN terminal.



## 6 Disclaimer

Monolithic Power Systems (MPS) reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. MPS makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

MPS cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an MPS product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage (“Critical Applications”).

MPS PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of MPS products in critical applications is understood to be fully at the risk of the customer.

Questions concerning potential risk applications should be directed to MPS.

MPS semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.



## REVISION HISTORY

Revision #	Revision Date	Description	Pages Updated
1.0	5/11/2020	Initial Release	-
1.1	6/15/2020	Updated BOM and updated images	2, 8-11
1.11	10/14/2020	Grammar and formatting updates	9–11, 13